

I completed this assignment entirely on my own.

Finite-state Machine \rightarrow simple vending machine

1) Run examples

$NNG \rightarrow G$

$DG \rightarrow G$

$NNNC \rightarrow C$

$NDC \rightarrow C$

$NNNG \rightarrow N, G$

$DNNG \rightarrow N, N, G$

$DC \rightarrow D$

$NG \rightarrow N$

2) states: how much \$ is in the vending machine (up to 15¢)

inputs: N = nickel

D = dime

G = request gum

C = request candy


outputs: O_N = nickel

O_D = dime


O_G = gum

O_C = candy

3) state diagram

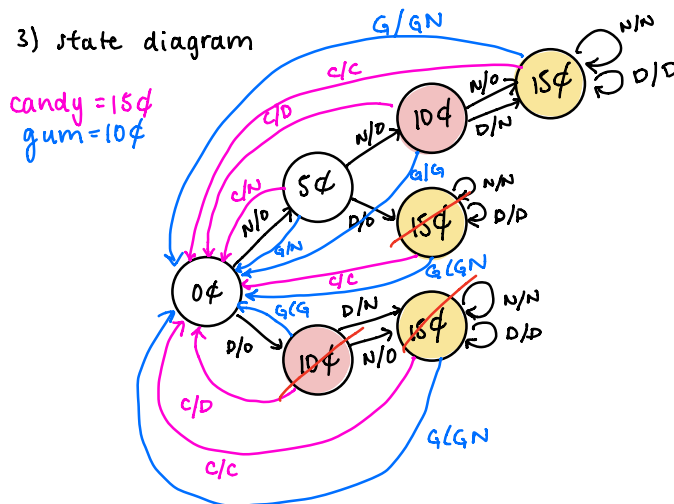

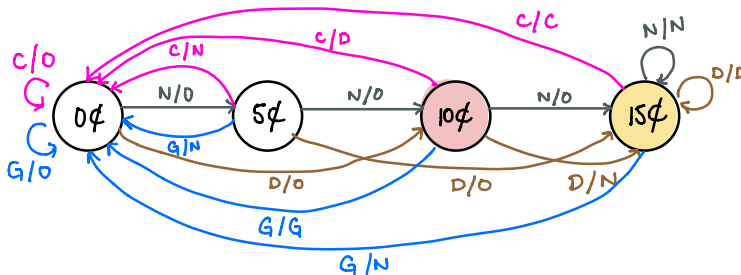4) state reduction - don't need to keep track of different inputs to get to same state!



to reduce states:

- 2 nickels = 1 dime
- 3 nickels = 1 dime + 1 nickel
- max \$ = 15¢
(don't care about values >)
- reduce 4 input to 2 bit input

5) state assignment:

FF A = Dime
FF B = Nickel

state	FF A	FF B
0¢	0	0
5¢	0	1
10¢	1	0
15¢	1	1

Inputs:


- coin input:

- nickel = 00
- dime = 01
- gum = 10
- candy bar = 11

- need encoder for 4 to 2 bits

input	I ₁	I ₀
N	0	0
D	0	1
G	1	0
C	1	1

4 to 2 encoder

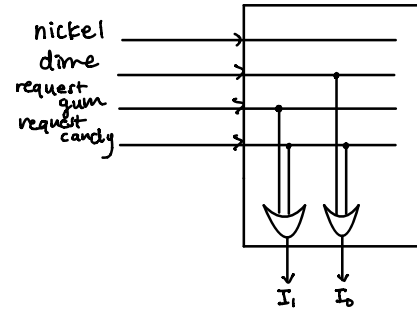

6) J-K flip flops (edge-triggered)

7) full-state table & flip-flop excitation table

J-K flip flop
Excitation Table

Q _t	Q _{t+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

state	current state		input		next state		(D) FF A		(N) FF B		output			
	A	B	I ₁	I ₀	A	B	J _A	K _A	J _B	K _B	dime O _b	nickel O _a	gum O _g	candy O _c
0¢	0	0	0	0	0	1	0	x	1	x	0	0	0	0
0¢	0	0	0	1	1	0	1	x	0	x	0	0	0	0
0¢	0	0	1	0	0	0	0	x	0	x	0	0	0	0
0¢	0	0	1	1	0	0	0	x	0	x	0	0	0	0
5¢	0	1	0	0	1	0	1	x	x	1	0	0	0	0
5¢	0	1	0	1	1	1	1	x	x	0	0	0	0	0
5¢	0	1	1	0	0	0	0	x	x	1	0	1	0	0
5¢	0	1	1	1	0	0	0	x	x	1	0	1	0	0
10¢	1	0	0	0	1	1	x	0	1	x	0	0	0	0
10¢	1	0	0	1	1	1	x	0	1	x	0	1	0	0
10¢	1	0	1	0	0	0	x	1	0	x	0	0	1	0
10¢	1	0	1	1	0	0	x	1	0	x	0	0	1	0
15¢	1	1	0	0	1	1	x	0	x	0	0	1	0	0
15¢	1	1	0	1	1	1	x	0	x	0	0	1	0	0
15¢	1	1	1	0	0	0	x	1	x	1	0	1	1	0
15¢	1	1	1	1	0	0	x	1	x	1	0	1	1	1

8) K-maps

- Flip-Flops:

N			
D	X	X	X
	X	X	X
	0	0	0
	1	1	1
I ₀			

$$JA = BI_1' + B'I_1'I_0$$

$$JA = I_1'(B + B'I_0)$$

N			
D	0	0	0
	1	1	1
	X	X	X
	X	X	X
I ₀			

$$KA = I_1$$

N			
D	X	X	1
	X	X	0
	X	X	0
	X	X	1
I ₀			

$$JB = AI_1' + A'I_1'I_0'$$

$$JB = I_1'(A + A'I_0')$$

N			
D	0	0	X
	1	1	X
	1	1	X
	1	0	X
I ₀			

$$KB = I_1 + A'I_1'I_0'$$

- Outputs:

By inspection:

$$O_D = AB'I_1I_0 + ABI_1'I_0$$

$$O_D = AI_0(B'I_1 + BI_1')$$

N			
D	1	0	1
	1	0	0
	1	1	0
	0	0	0
I ₀			

$$O_N = ABI_0' + A'B'I_1 + AB'I_1'I_0$$

$$O_N = B(AI_0' + A'I_1) + AB'I_1'I_0$$

By inspection:


$$O_G = AB'I_1I_0' + ABI_1I_0'$$

$$O_G = AI_1I_0'(B' + B)$$

$$O_G = AI_1I_0'$$

$$O_C = ABI_1I_0$$

9) circuit diagram

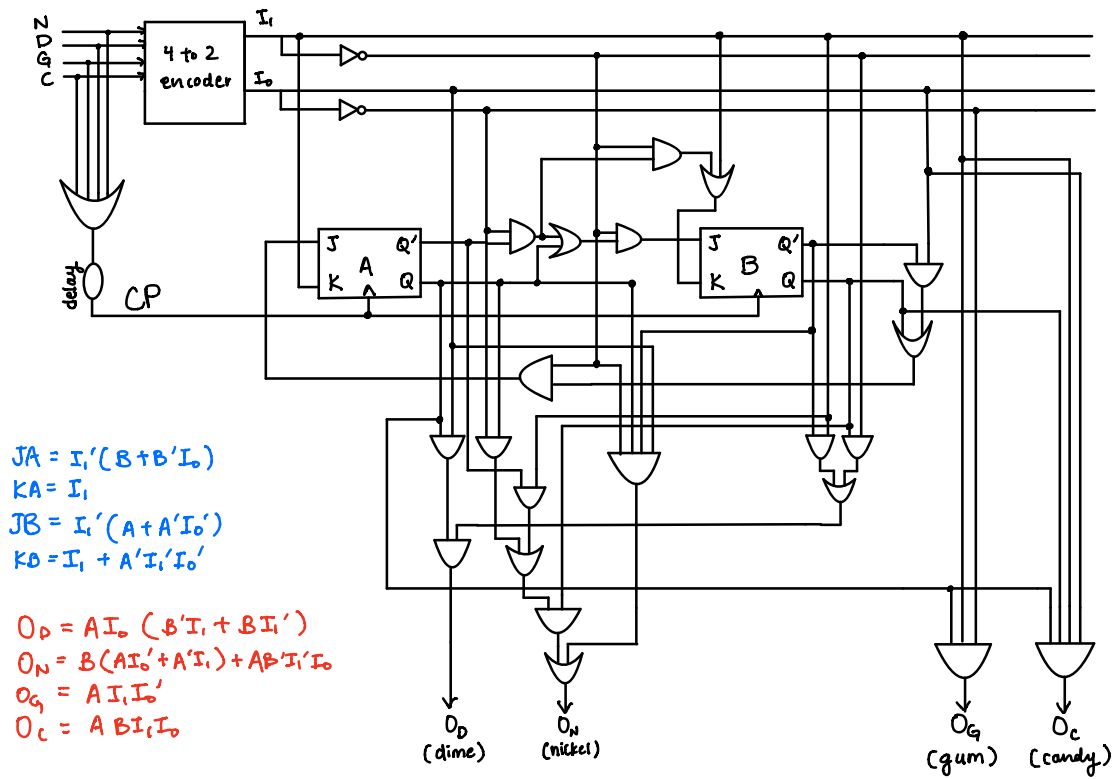

10) unused states

- there are no unused states as we cover all $2^4 = 16$ possible states.